

Quantum Computation


Quantum Circuits Activity

Francisco Vazquez-Tavares

November 3, 2025

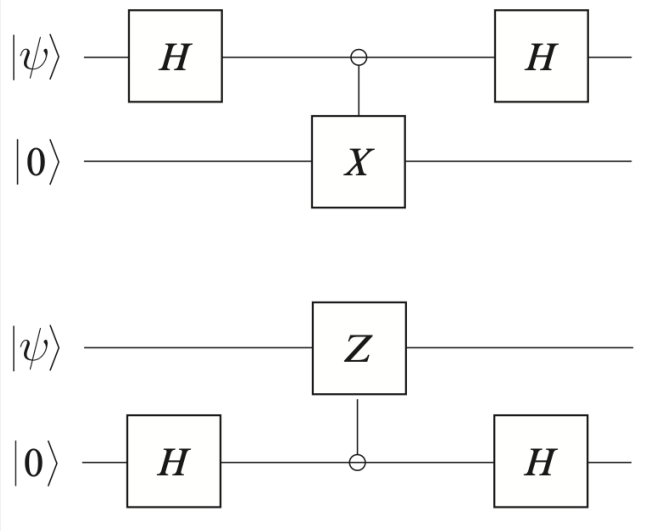Problem 1:

Compare the effect of the following two circuits



Let's consider the following general state $|\psi\rangle = a|0\rangle + b|1\rangle$ with $a, b \in \mathbb{C}$. The first circuit can be represented with the following algebraic expression

$$[(\hat{H} \otimes \mathbb{1}) (\Lambda \hat{X}) (\hat{H} \otimes \mathbb{1})] (|\psi\rangle \otimes |0\rangle).$$

Where $\Lambda \hat{X}$ denotes the controlled \hat{X} gate ($|0\rangle\langle 0| \otimes \mathbb{1} + |1\rangle\langle 1| \otimes \hat{X}$), \hat{H} is the Haddamard gate and \hat{X} is the X gate.

Starting with the first gate,

$$\begin{aligned} (\hat{H} \otimes \mathbb{1}) (|\psi\rangle \otimes |0\rangle) &= \hat{H} |\psi\rangle \otimes \mathbb{1} |0\rangle \\ &= \left[\frac{a}{\sqrt{2}}(|0\rangle + |1\rangle) + \frac{b}{\sqrt{2}}(|0\rangle - |1\rangle) \right] \otimes \mathbb{1} |0\rangle \\ &= \left[\frac{(a+b)}{\sqrt{2}} |0\rangle + \frac{(a-b)}{\sqrt{2}} |1\rangle \right] \otimes \mathbb{1} |0\rangle \\ &= \frac{(a+b)}{\sqrt{2}} |00\rangle + \frac{(a-b)}{\sqrt{2}} |10\rangle. \end{aligned}$$

Now we compute the controlled \hat{X} gate with the new state with the following mnemonic rule, *It flips the second qubit if the first qubit is 1 and leaves unchanged otherwise*, therefore

$$\Lambda \hat{X} \left[\frac{(a+b)}{\sqrt{2}} |00\rangle + \frac{(a-b)}{\sqrt{2}} |10\rangle \right] = \frac{(a+b)}{\sqrt{2}} |00\rangle + \frac{(a-b)}{\sqrt{2}} |11\rangle = |\psi_2\rangle.$$

Finally, we apply the last Haddamard gate into the nwe state,

$$\begin{aligned}
 (\hat{H} \otimes \mathbb{1}) |\psi_2\rangle &= \frac{(a+b)}{\sqrt{2}} \hat{H} |0\rangle \otimes \mathbb{1} |0\rangle + \frac{(a-b)}{\sqrt{2}} \hat{H} |1\rangle \otimes \mathbb{1} |1\rangle \\
 &= \frac{(a+b)}{\sqrt{2}} \left(\frac{1}{\sqrt{2}} (|0\rangle + |1\rangle) \right) \otimes \mathbb{1} |0\rangle + \frac{(a-b)}{\sqrt{2}} \left(\frac{1}{\sqrt{2}} (|0\rangle - |1\rangle) \right) \otimes \mathbb{1} |1\rangle \\
 &= \frac{(a+b)}{2} (|00\rangle + |10\rangle) + \frac{(a-b)}{2} (|01\rangle - |11\rangle).
 \end{aligned}$$

After expanding the expression and minor algebraic manipulations we can express the final state in terms of the of the Bell states,

$$(\hat{H} \otimes \mathbb{1}) |\psi_2\rangle = \frac{a}{\sqrt{2}} (|\Psi^+\rangle + |\Phi^+\rangle) + \frac{b}{\sqrt{2}} (|\Psi^+\rangle - |\Phi^-\rangle)$$

Now let's compute the final state in the second circuit to compare it with the previous result. First we state th algebraic representation of the circuit as follows,

$$[(\mathbb{1} \otimes \hat{H}) (\hat{Z} \Lambda) (\mathbb{1} \otimes \hat{H})] (|\psi\rangle \otimes |0\rangle).$$

Where $\hat{Z} \Lambda$ denotes the controlled \hat{Z} gate ($\mathbb{1} \otimes |0\rangle\langle 0| + \hat{Z} \otimes |1\rangle\langle 1|$), \hat{H} is the Haddamard gate and \hat{Z} is the Z gate.

Let's begin with the first gate,

$$\begin{aligned}
 |\psi_2\rangle &= (\mathbb{1} \otimes \hat{H}) (|\psi\rangle \otimes |0\rangle) \\
 &= \mathbb{1} |\psi\rangle \otimes \hat{H} |0\rangle \\
 &= (a |0\rangle + b |1\rangle) \otimes \left(\frac{1}{\sqrt{2}} (|0\rangle + |1\rangle) \right) \\
 &= a |0\rangle \otimes \left(\frac{1}{\sqrt{2}} (|0\rangle + |1\rangle) \right) + b |1\rangle \otimes \left(\frac{1}{\sqrt{2}} (|0\rangle + |1\rangle) \right) \\
 &= \frac{a}{\sqrt{2}} (|00\rangle + |01\rangle) + \frac{b}{\sqrt{2}} (|10\rangle + |11\rangle).
 \end{aligned}$$

The next step is to compute the controlled \hat{Z} gate into the new state,

$$\hat{Z} \Lambda |\psi_2\rangle = (\mathbb{1} \otimes |0\rangle\langle 0| + \hat{Z} \otimes |1\rangle\langle 1|) \left(\frac{a}{\sqrt{2}} (|00\rangle + |01\rangle) + \frac{b}{\sqrt{2}} (|10\rangle + |11\rangle) \right)$$

$$\begin{aligned}
 \hat{Z} \Lambda |\psi_2\rangle &= \left[\frac{a}{\sqrt{2}} (\mathbb{1} \otimes |0\rangle\langle 0|) (|00\rangle + |01\rangle) + \frac{b}{\sqrt{2}} (\mathbb{1} \otimes |0\rangle\langle 0|) (|10\rangle + |11\rangle) \right. \\
 &\quad \left. + \frac{a}{\sqrt{2}} (\hat{Z} \otimes |1\rangle\langle 1|) (|00\rangle + |01\rangle) + \frac{b}{\sqrt{2}} (\hat{Z} \otimes |1\rangle\langle 1|) (|10\rangle + |11\rangle) \right]
 \end{aligned}$$

$$\begin{aligned}\hat{Z}\Lambda|\psi_2\rangle = & \left[\frac{a}{\sqrt{2}} ((\mathbb{1}|0\rangle \otimes |0\rangle\langle 0| |0\rangle) + (\mathbb{1}|0\rangle \otimes |0\rangle\langle 0| |1\rangle)) \right. \\ & + \frac{b}{\sqrt{2}} ((\mathbb{1}|1\rangle \otimes |0\rangle\langle 0| |0\rangle) + (\mathbb{1}|1\rangle \otimes |0\rangle\langle 0| |1\rangle)) \\ & + \frac{a}{\sqrt{2}} ((\hat{Z}|0\rangle \otimes |1\rangle\langle 1| |0\rangle) + (\hat{Z}|0\rangle \otimes |1\rangle\langle 1| |1\rangle)) \\ & \left. + \frac{b}{\sqrt{2}} ((\hat{Z}|1\rangle \otimes |1\rangle\langle 1| |0\rangle) + (\hat{Z}|1\rangle \otimes |1\rangle\langle 1| |1\rangle)) \right]\end{aligned}$$

$$\begin{aligned}\hat{Z}\Lambda|\psi_2\rangle = & \left[\frac{a}{\sqrt{2}} ((\mathbb{1}|0\rangle \otimes |0\rangle) + (\mathbb{1}|0\rangle \otimes |\emptyset\rangle)) \right. \\ & + \frac{b}{\sqrt{2}} ((\mathbb{1}|1\rangle \otimes |0\rangle) + (\mathbb{1}|1\rangle \otimes |\emptyset\rangle)) \\ & + \frac{a}{\sqrt{2}} ((\hat{Z}|0\rangle \otimes |\emptyset\rangle) + (\hat{Z}|0\rangle \otimes |1\rangle)) \\ & \left. + \frac{b}{\sqrt{2}} ((\hat{Z}|1\rangle \otimes |\emptyset\rangle) + (\hat{Z}|1\rangle \otimes |1\rangle)) \right]\end{aligned}$$

$$\begin{aligned}\hat{Z}\Lambda|\psi_2\rangle = & \left[\frac{a}{\sqrt{2}} ((\mathbb{1}|0\rangle \otimes |0\rangle)) \right. \\ & + \frac{b}{\sqrt{2}} ((\mathbb{1}|1\rangle \otimes |0\rangle)) + \frac{a}{\sqrt{2}} ((\hat{Z}|0\rangle \otimes |1\rangle)) \\ & \left. + \frac{b}{\sqrt{2}} ((\hat{Z}|1\rangle \otimes |1\rangle)) \right]\end{aligned}$$

$$\hat{Z}\Lambda|\psi_2\rangle = \frac{a}{\sqrt{2}}(|00\rangle + |11\rangle) + \frac{b}{\sqrt{2}}(|10\rangle + |01\rangle) = |\psi_3\rangle$$

Finally, with the new state we can compute the last Haddamard gate in order to compare the result with the previous one,

$$\begin{aligned}(\mathbb{1} \otimes \hat{H})|\psi_3\rangle &= (\mathbb{1} \otimes \hat{H}) \left(\frac{a}{\sqrt{2}}(|00\rangle + |11\rangle) + \frac{b}{\sqrt{2}}(|10\rangle + |01\rangle) \right) \\ &= \left(\frac{a}{\sqrt{2}} (\mathbb{1} \otimes \hat{H}) (|00\rangle + |11\rangle) + \frac{b}{\sqrt{2}} (\mathbb{1} \otimes \hat{H}) (|10\rangle + |01\rangle) \right) \\ &= \left(\frac{a}{2}(|00\rangle + |01\rangle + |10\rangle - |11\rangle) + \frac{b}{2}(|10\rangle + |11\rangle + |00\rangle - |01\rangle) \right) \\ &= \frac{a}{\sqrt{2}} (|\Psi^-\rangle + |\Phi^+\rangle) + \frac{b}{\sqrt{2}} (|\Psi^+\rangle + |\Phi^-\rangle)\end{aligned}$$

Now that we have the final state of the second circuit we can compare both results,


$$\text{First circuit } |\psi_0\rangle \rightarrow \frac{a}{\sqrt{2}} (|\Psi^+\rangle + |\Phi^+\rangle) + \frac{b}{\sqrt{2}} (|\Psi^+\rangle - |\Phi^-\rangle)$$

$$\text{Second circuit } |\psi_0\rangle \rightarrow \frac{a}{\sqrt{2}} (|\Psi^-\rangle + |\Phi^+\rangle) + \frac{b}{\sqrt{2}} (|\Psi^+\rangle + |\Phi^-\rangle).$$

In both cases we can see how the states transform from a computational basis to a linear combination of the Bell states basis. That can be interpreted as that this circuit transforms a state to a linear combination of entangled states. On the other hand, we can see that the main difference between both circuits is that change in sign on the second term of the linear combination and the change of the Bell state in the first term.

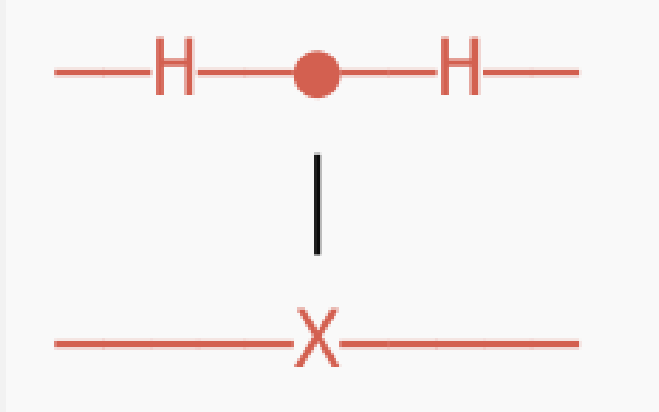Problem 2:

Show that the following quantum circuit is equivalent to a controlled Z-gate



Let's start by computing the result of the controlled Z gate in the two qubit system $|\psi\rangle \otimes |0\rangle$, where $|\psi\rangle$ is a general state $|\psi\rangle = a|0\rangle + b|1\rangle$,

$$\begin{aligned} \Lambda \hat{Z} |\psi 0\rangle &= (|0\rangle\langle 0| \otimes \mathbb{1} + |1\rangle\langle 1| \otimes \hat{Z}) (a|00\rangle + b|10\rangle) \\ &= (|0\rangle\langle 0| \otimes \mathbb{1}) (a|00\rangle + b|10\rangle) + (|1\rangle\langle 1| \otimes \hat{Z}) (a|00\rangle + b|10\rangle) \\ &= a|00\rangle + b|10\rangle. \end{aligned}$$

Now it is time to compute the circuit shown in the previous figure. Let's begin with the first Haddamard gate,

$$\begin{aligned} (\hat{H} \otimes \mathbb{1}) |\psi 0\rangle &= a(\hat{H} \otimes \mathbb{1}) |00\rangle + b(\hat{H} \otimes \mathbb{1}) |10\rangle \\ &= a \left(\frac{1}{\sqrt{2}} (|00\rangle + |10\rangle) \right) + b \left(\frac{1}{\sqrt{2}} (|00\rangle - |10\rangle) \right) \\ &= \frac{a+b}{\sqrt{2}} |00\rangle + \frac{a-b}{\sqrt{2}} |10\rangle. \end{aligned}$$

Now, we can applied the controlled \hat{X} gate,

$$\begin{aligned} \Lambda \hat{Z} (\hat{H} \otimes \mathbb{1}) |\psi 0\rangle &= (|0\rangle\langle 0| \otimes \mathbb{1} + |1\rangle\langle 1| \otimes \hat{Z}) \left(\frac{a+b}{\sqrt{2}} |00\rangle + \frac{a-b}{\sqrt{2}} |10\rangle \right) \\ &= (|0\rangle\langle 0| \otimes \mathbb{1}) \left(\frac{a+b}{\sqrt{2}} |00\rangle + \frac{a-b}{\sqrt{2}} |10\rangle \right) + (|1\rangle\langle 1| \otimes \hat{Z}) \left(\frac{a+b}{\sqrt{2}} |00\rangle + \frac{a-b}{\sqrt{2}} |10\rangle \right) \\ &= \frac{a+b}{\sqrt{2}} |00\rangle + \frac{a-b}{\sqrt{2}} |10\rangle \end{aligned}$$

To finish, let's apply the last Haddamard gate,

$$\begin{aligned} (\hat{H} \otimes \mathbb{1}) \left(\frac{a+b}{\sqrt{2}} |00\rangle + \frac{a-b}{\sqrt{2}} |10\rangle \right) &= \frac{a+b}{\sqrt{2}} \left(\frac{1}{\sqrt{2}} (a|00\rangle + b|10\rangle) \right) + \frac{a-b}{\sqrt{2}} \left(\frac{1}{\sqrt{2}} (a|00\rangle - b|10\rangle) \right) \\ &= \frac{a+b}{2} (a|00\rangle + b|10\rangle) + \frac{a-b}{2} (a|00\rangle - b|10\rangle) \\ &= a^2 |00\rangle + (b^2 + ab) |10\rangle. \end{aligned}$$

We can see that this circuit is not equivalent as claimed in the exercise. On the other hand, if we change the circuit by swapping the controlled \hat{X} gate to the \hat{X} gate, the result is equivalent to applying a controlled \hat{Z} gate. Let's resume from the first Haddamard gate,

$$(\hat{X} \otimes \mathbb{1}) \left(\frac{a+b}{\sqrt{2}} |00\rangle + \frac{a-b}{\sqrt{2}} |10\rangle \right) = \left(\frac{a+b}{\sqrt{2}} |10\rangle + \frac{a-b}{\sqrt{2}} |00\rangle \right).$$

Now, let's finish by applying the last Haddamard gate,

$$\begin{aligned} (\hat{H} \otimes \mathbb{1}) \left(\frac{a+b}{\sqrt{2}} |10\rangle + \frac{a-b}{\sqrt{2}} |00\rangle \right) &= \left(\frac{a+b}{\sqrt{2}} \frac{1}{\sqrt{2}} (|00\rangle - |10\rangle) \right) + \left(\frac{a-b}{\sqrt{2}} \frac{1}{\sqrt{2}} (|00\rangle + |10\rangle) \right) \\ &= \left(\frac{a+b}{2} (|00\rangle - |10\rangle) \right) + \left(\frac{a-b}{2} (|00\rangle + |10\rangle) \right) \\ &= a |00\rangle - b |10\rangle. \end{aligned}$$

If we only focus in the first term we get the same as the controlled \hat{Z} gate, however we get a sign difference in the second term.


Problem 3:

The three qubit GHZ-state is defined as

$$|GHZ\rangle = \frac{1}{2}(|000\rangle + |111\rangle).$$

Design a circuit that upon of the separable state $|000\rangle$ constructs the GHZ-state.

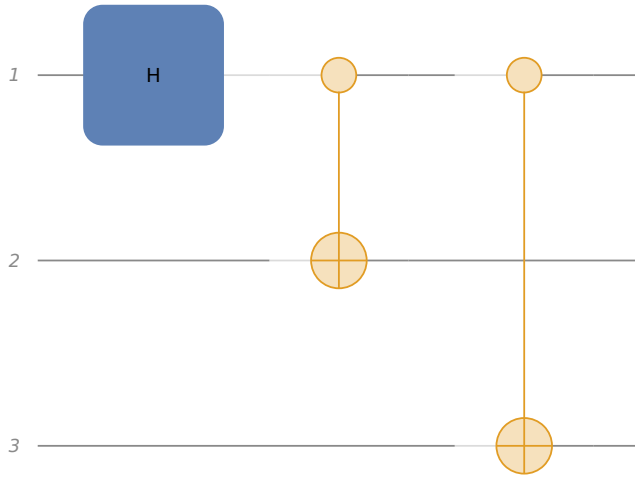For this last problem, it is implemented the following circuit,



Let's start by computing the first Haddamard gate,

$$(\hat{H} \otimes \mathbb{1} \otimes \mathbb{1}) |000\rangle = \frac{1}{\sqrt{2}}(|000\rangle + |100\rangle).$$

Now, lets apply the first controlled \hat{X} gate,

$$(\Lambda \otimes \hat{X} \otimes \mathbb{1}) \frac{1}{\sqrt{2}}(|000\rangle + |100\rangle) = \frac{1}{\sqrt{2}}(|000\rangle + |110\rangle).$$

Now, lets finish with the second controlled \hat{X} gate,

$$(\Lambda \otimes \mathbb{1} \otimes \hat{X}) \frac{1}{\sqrt{2}}(|000\rangle + |110\rangle) = \frac{1}{\sqrt{2}}(|000\rangle + |111\rangle).$$

It is missed the factor of $1/2$, however due to time constrictions I could not explore more circuits and this circuit was the one that give the nearest result. To get the factor of $1/2$ my intuition guide my to apply two haddamard gates, however, the process to eliminate the cross terms is overwhelming and could not find a circuit that gives the require state.